



CSE 313s

Selected Topics in Computer Engineering

Sheet 3

1. What is coverage?
2. What is the meaning of code coverage?
3. What is a coverage driven verification?
4. What is the difference between X and Z in verilog?
5. Which coverage has more importance, code coverage or functional coverage?
6. What is the difference between the following two declarations?

```
1 wire [7:0] w1;  
2 wire [0:7] w2;
```

7. What is 10'had?
8. Write a Verilog behavioral description of a four-bit adder module. The adder should have three inputs, *a*, *b*, and *c_{in}*, and two outputs, *sum* and *c_{out}*. Ports *c_{in}* and *c_{out}* are one bit, the other ports are four bits each.
9. Write a Verilog structural description of an eight-bit adder that uses two of the four-bit adders of the previous problem. (That is, instantiate the modules designed in the previous problem)
10. An accumulator has three inputs, *amt*, *reset*, and *clk*, and an output, *sum*. The accumulator has an internal 32-bit register which is updated as follows:
 - On a positive edge of *clk* it adds *amt*, a 32-bit integer, to the register;
 - On the negative edge of *clk* it places the new *sum* on its outputs (until the next negative edge).
 - Whenever *reset* is high the register is set to zero and the output changes immediately.Write a Verilog behavioral description of this module.

11. The code below starts executing at $t = 0$. Show all changes in a , include the time of the change and the new value.

```

1 integer a;
2 initial begin
3   a = 1;
4   #1;
5   a = 2;
6   #1;
7   a = 3;
8   #1;
9   a <= 4;
10  #1;
11  a <= 5;
12  #1;
13  #3 a = a+1;
14  #1;
15  a = #3 a+1;
16  #1;
17  a <= #3 a+1;
18  #1;
19  a = a+1;
20 end

```

12. The programmer expected execution to exit the loop below when either i was 1000 or $a[i] == c$, but that's not what happened. What goes wrong and how can it be fixed? The loop must be exited using a *disable* statement.

```

1 integer i, c;
2 integer a[0:999];
3
4 // ...
5 i = 0;
6 while( i < 1000 ) begin:LOOP
7   if( a[i] == c ) disable LOOP;
8   i = i + 1;
9 end

```

13. For the Verilog code segment below, which of the lines implement a shift register?

```

1 always@ (posedge clk)
2   begin
3     z = y; y = x;
4     y1= x1; z1 = y1;
5     z2<= y2; y2 <= x2;
6     y3<= x3; z3 <= y3;

```

14. If a variable is not assigned in all possible executions of an always statement then:
- A don't care is inferred
 - A latch is inferred
 - The variable is set to 0
 - The synthesis process will fail
15. An entry level engineer has implemented Verilog code with the objective of designing a counter that continuously counts down from 7 to 0 in binary and then back to 7 again (counts 111, 110, 101, ..., 000, 111, 110, 101, ...). Unfortunately, the designer made a number of mistakes in the design. Please fix all the bugs using minimal changes. The counter bits are: c3 c2 c3 (Assume c3 is the most significant bit)

```

1 module top(clk, r, c1, c2, c3);
2   input r, clk;
3   output c1, c2, c3;
4   reg c1, c2, c3;
5
6   assign x = 1'b1;
7   my_unit u1(clk, r, x, x, c1);
8   my_unit u2(clk, r, c1, x, c2);
9   my_unit u3(clk, r, x, c2, c3);
10 endmodule
11
12 module my_unit(clk,r,a,b,c);
13   input clk,r,a,b;
14   output c;
15   reg c;
16
17   always@(negedge clk)
18     c <= (~a&~c) | ((~b)&c);
19
20   always@(r) c <= 1'b0;
21 endmodule

```


16. A recognizer has one input "X" and one output "Y". At each clock cycle, the input "X" value is read. When a sequence of "101" is observed in the input sequence, the output, "Y", will become 1, otherwise it will be 0.
- Draw Moore state machine diagram with minimum number of states.
 - Write the Verilog representation of your Moore state machine.
17. Use the following Verilog module to answer the question below:

```

1 module my_unit(clk, x, y1, y2);
2   input clk, x;
3   output y1, y2;
4   reg y1, y2;
5   wire w;
6
7   assign w = x|(~y1);
8   always@(posedge clk)
9     y2 <= w;
10
11   always@(negedge clk)
12     y1 <= y2;
13 endmodule

```

 - a. Draw the output waveforms for the specified inputs.



- b. Draw the logic diagram for the circuit that represents **my_unit**

18. Your job is to design a 3-bit ALU for the specifications in the table below. This unit has a two bit control lines ($P_1 P_0$), to select the required operation, and 3-bit input data $D[2:0]$. The output lines are $Q[2:0]$.

| $P_1 P_0$ | Operation |
|-----------|---|
| 0 0 | $Q = D$ |
| 0 1 | $Q = Q'$ (New Q is the complement of the current Q) |
| 1 0 | $Q = 2Q$ (New Q is twice the current Q) |
| 1 1 | $Q = 2Q + 1$ (New Q is twice the current Q plus 1) |