

Tutorial 3

CSE 313

Modules

```
Module Module_name ( input wire [1:0] x, output reg [3:0] y);  
    //code  
endmodule
```

Or

```
Module Module_name ( x, y);  
Input x;  
Output y;  
wire [1:0] x;  
reg[3:0] y;  
    //code  
endmodule
```

Blocks

```
always @ ( posedge clk or negedge rst)
begin
    //code
end
```

```
Initial
begin
    //code
end
```

Data types

- Nets
 - Ex: Wire, tri, wand, supply0
 - Can only be in continuous assignments (using assign keyword)
 - continuous assignments exists in parallel domains (modules)
- Variables
 - Ex: reg, int, string
 - Can only be in procedural assignments
 - procedural assignments exists in sequential domains (blocks)
- Testbench variables
 - Ex: logic, bit
 - Exist anywhere


MSB rules

What is the difference between the following two declarations?

```
1 wire [7:0] w1;  
2 wire [0:7] w2;
```

What is 10'had?

Port type rules

 

Blocking and non-blocking (procedural assignments)

. The code below starts executing at $t = 0$. Show all changes in a , include the time of the change and the new value.

```
1 integer a;  
2 initial begin  
3   a = 1;  
4   #1;  
5   a = 2;  
6   #1;  
7   a = 3;  
8   #1;  
9   a <= 4;  
10  #1;  
11  a <= 5;  
12  #1;  
13  #3 a = a+1;  
14  #1;  
15  a = #3 a+1;  
16  #1;  
17  a <= #3 a+1;  
18  #1;  
19  a = a+1;  
20 end
```

Behavioral VS structural design

Write a Verilog behavioral description of a four-bit adder module. The adder should have three inputs, a, b, and c_{in} , and two outputs, sum and cout. Ports c_{in} and c_{out} are one bit, the other ports are four bits each.

```
1 module add4(sum,cout, a, b, cin);
2   output sum, cout;
3   input a, b, cin;
4
5   reg [3:0] sum;
6   reg cout;
7   wire [3:0] a, b;
8   wire cin;
9
10  always @( a or b or cin ) {cout,sum} =a+b+ cin;
11 endmodule // add4
```

```
module full_adder ( a ,b ,c ,sum ,carry );
output sum ;
output carry ;
input a ;
input b ;
input c ;

    assign sum = a ^ b ^ c;
    assign carry = (a&b) | (b&c) | (c&a);

endmodule
//-----
module adder_4bit ( a ,b ,sum ,carry );
output [3:0] sum ;
output carry ;
input [3:0] a ;
input [3:0] b ;

    wire [2:0] s;

    full_adder u0 (a[0],b[0],1'b0,sum[0],s[0]);
    full_adder u1 (a[1],b[1],s[0],sum[1],s[1]);
    full_adder u2 (a[2],b[2],s[1],sum[2],s[2]);
    full_adder u3 (a[3],b[3],s[2],sum[3],carry);

endmodule
```


Lab 1

.An accumulator has three inputs, *amt*, *reset*, and *clk*, and an output, *sum*. The accumulator has an internal 32-bit register which is updated as follows:

- On a positive edge of *clk* it adds *amt*, a 32-bit integer, to the register;
- On the negative edge of *clk* it places the new *sum* on its outputs (until the next negative edge).
- Whenever *reset* is high the register is set to zero and the output changes immediately.

Write a Verilog behavioral description of this module.